

Figure 1: Waveforms from testbench, visualised by GTKWave

 


Figure 2: Clean waveforms

 


Figure 3: Logic gate circuit

```

c <= a and b;
d <= a nor b;
e <= a and not b;
f <= b and not a;
dir <= dir_n nor e;
dir_n <= dir nor f;
pul <= pul_n nor d;
pul_n <= pul nor c;
pulse <= pul;
direction <= dir;

```

Figure 4: VHDL code

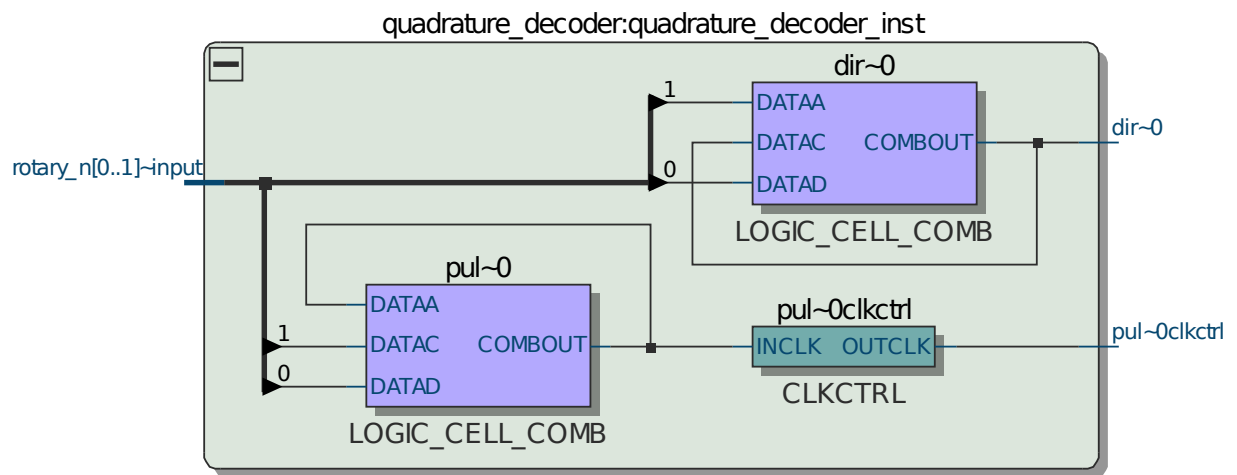


Figure 5: Reduced to two logic elements by Altera Quartus